

Analogue Integrated Circuits Report

Fergal Lonergan 13456938

Lab 2

Introduction to choices for design parameters.

Why use g_m/I_d as a design parameter?

$$\frac{W}{L} = \frac{g_m}{\mu C_{ox} V_{ov}}$$

With our g_m and L fixed, smaller V_{ov} translates to a bigger (wider) device and a larger unwanted C_{gs} .

Therefore V_{ov} isn't a good design parameter for our MOSFET so we use g_m/I_d .

g_m/I_d is relevant for three reasons:

1. Strongly related to the performance of your analog circuit.
2. Gives a good indication of our device's operation region.
3. Provides a tool for calculating our transistor dimensions $\frac{W}{L}$.

How does it indicate our mode of operation?

$$\frac{g_m}{I_d} = \frac{1}{I_d} \left(\frac{\partial I_d}{\partial V_g} \right) = \frac{\partial (\ln I_d)}{\partial V_g} = \frac{\partial \left\{ \ln \left[\frac{I_d}{\frac{W}{L}} \right] \right\}}{\partial V_g}$$

So our derivative is max in the inversion region. $\frac{g_m}{I_d}$ ratio decreases as the operating point moves towards strong inversion.

What do we want from our transistor?

- Large g_m without investing too much current I_d
- Large g_m without a large C_{gs}

What performance metrics do we use?

- Transit frequency or Unity gain frequency
 $\omega_T = \frac{g_m}{C_{gs}}$ Max frequency for which our MOSFET acts like an amplifier.
- Intrinsic gain
 $g_m r_o$
- Transconductor efficiency (Want this to be Large)


$$\frac{g_m}{I_d}$$

Ability to translate current to transconductance.

Lab work

The aim of our lab was to simulate 180nm TSMC MOSFETs by using simulations in Cadence ADE, and then to characterise a MOSFET by choosing appropriate design parameters to meet our specifications provided.

NMOS VSTAR TABLE

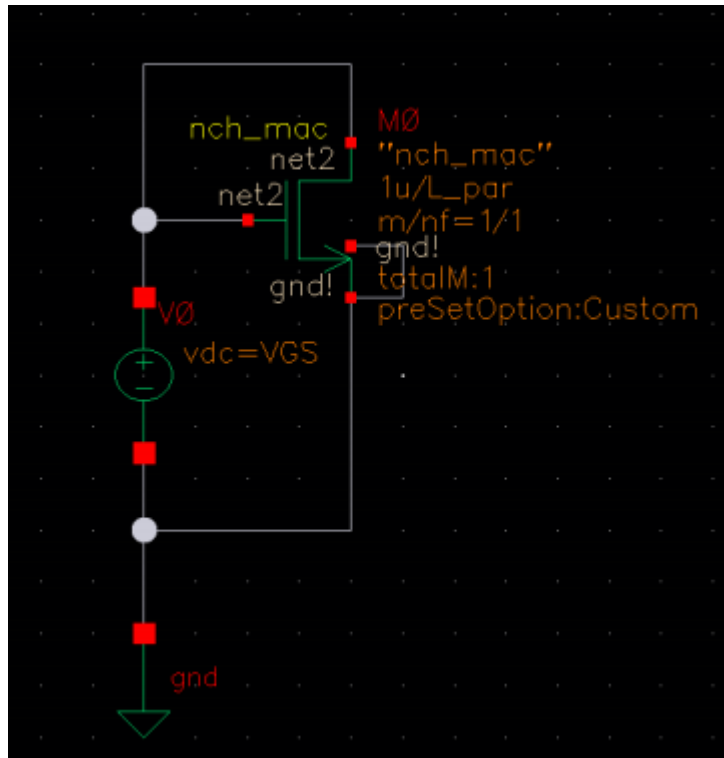

Our circuit consisted of a single NMOS TSMC MOSFET with its' bulk shorted to its' source which was set to ground. Our gate and drain are then set to a value V_{dc} from a voltage source which is at 1.8V. We then ran a DC analysis of the circuit at an operating point of 100mV and used the simulation to produce the following values.

Name/Signal/Expr	Value	Plot	Save	Save Option
1 gm_id	28.4245	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
2 fT	799.997K	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
3 gm_id_fT	22.7395M	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
4 Vstar	70.3618m	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
5 Istar	69.0314u	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	

Plot after simulation: Plotting mode:

Status: Ready | T=27 C | Simulator: spectre

For $L = 200nm$

Our equations are:

$$gm_{id} = \frac{gm}{I_d}$$

$$fT = \frac{gm}{C_{gs} 2\pi}$$

$$gm_{id} fT = \frac{gm}{(\frac{I_d}{fT})}$$

$$V_{star} = \frac{2}{\frac{gm}{I_d}}$$

$$I_{star} = \frac{I_d}{W}$$

Our analysis swept the Vdc voltage source from 0.1V-1.8V, and then swept the transistor length from 200nm-1000nm.

Analysing the Graphs

Values for L (Mosfet Length):

- Red = 200nm
- Yellow = 400nm
- Green = 600nm
- Light Blue = 800nm
- Dark Blue = 1um

gm_{id}

Graph 1

At lower values of Vgs, our circuit has a much greater Transconductor efficiency. This is where our circuit has weak to moderate inversion. We also notice that varying the channel length has very little effect on this property.

f_t

Graph 2

As our channel length decreases our transit frequency increases. Therefore shorter transistors are considered faster and can “switch” their voltage quicker. Furthermore if we increase the value of Vgs this will increase our transit frequency. We notice in particular that when Vgs is larger than 0.4-0.5V that the transit frequency rises quite rapidly. I think it is fair to assume that our threshold voltage lies around here.

$gm_{id} f_t$

Graph 3

This value is used to represent the average performance of a MOSFET. We can see that if you shorten your channel length you can vastly increase your MOSFET performance. Also the region of voltage Vgs for which the MOSFET performs best is between 0.5-1.25V, with the highest performance around 0.75V.

V_{star} (V overdrive)

Graph 4

V_{star} is equal to $V_{gs} - V_{th}$, so we see that once the value of V_{gs} exceeds our threshold, about 0.4V, That the relationship is practically linear. Our V_{star} relationship is also greater in MOSFETs with shorter channel length but this is only apparent when the value for V_{gs} becomes quite large.

Istar

Graph 5

This shows the relationship of our current I_d to our channel width. It increases when V_{gs} increases and when the channel length decreases.

NMOS IGAIN TABLE

This circuit was the same as before however there was now a fixed voltage of 0.91V on the gate. We then sweep V_{ds} from 100mV to 1.8V and again sweep our channel Length L from 200nm-1000nm.

GRAPH

g_{m_gds}

This graph shows that as our V_{ds} increases our Intrinsic gain increase accordingly. The relationship is almost linear once it becomes greater than 0.4-0.5V the Value of our threshold voltage. It is also clear that by increasing the length of your channel length L , you can achieve larger intrinsic gains. This mean that longer transistors are capable of amplifying greater.